

18-3 Ohm's Law: Resistance and Resistors

To produce an electric current in a circuit, a difference in potential is required. One way of producing a potential difference along a wire is to connect its ends to the opposite terminals of a battery. It was Georg Simon Ohm (1787–1854) who established experimentally that the current in a metal wire is proportional to the potential difference V applied to its two ends:

$$I \propto V.$$

If, for example, we connect a wire to a 6-V battery, the current in the wire will be twice what it would be if the wire were connected to a 3-V battery. It is also found that reversing the sign of the voltage does not affect the magnitude of the current.

Water analogy

A useful analogy compares the flow of electric charge in a wire to the flow of water in a river, or in a pipe, acted on by gravity. If the river or pipe is nearly level, the flow rate is small. But if one end is somewhat higher than the other, the flow rate—or current—is greater. The greater the difference in height, the swifter the current. We saw in Chapter 17 that electric potential is analogous, in the gravitational case, to the height of a cliff. This applies in the present case to the height through which the fluid flows. Just as an increase in height can cause a greater flow of water, so a greater electric potential difference, or voltage, causes a greater electric current.

Exactly how large the current is in a wire depends not only on the voltage, but also on the resistance the wire offers to the flow of electrons. The walls of a pipe, or the banks of a river and rocks in the middle, offer resistance to the current. Similarly, electron flow is impeded because of interactions with the atoms of the wire. The higher this resistance, the less the current for a given voltage V . We then define electrical *resistance* so that the current is inversely proportional to the resistance: that is,

$$R = \frac{V}{I} \quad (18-2a)$$

where R is the **resistance** of a wire or other device, V is the potential difference applied across the wire or device, and I is the current through it. Equation 18-2a is often written as

OHM'S "LAW"

$$V = IR. \quad (18-2b)$$

As mentioned above, Ohm found experimentally that in metal conductors R is a constant independent of V , a result known as **Ohm's law**. Equation 18-2b, $V = IR$, is itself sometimes called Ohm's law, but only when referring to materials or devices for which R is a constant independent of V . But R is not a constant for many substances other than metals, nor for devices such as diodes, vacuum tubes, transistors, and so on. Thus Ohm's "law" is not a fundamental law, but rather a description of a certain class of materials: metal conductors. Materials or devices that do not follow Ohm's law ($R = \text{constant}$) are said to be *nonohmic*. See Fig. 18-9.

Unit of electrical resistance: the ohm ($1 \Omega = 1 \text{ V/A}$)

The unit for resistance is called the **ohm** and is abbreviated Ω (Greek capital letter omega). Because $R = V/I$, we see that 1.0Ω is equivalent to 1.0 V/A .

FIGURE 18-9 Graphs of current vs. voltage for (a) a metal conductor which obeys Ohm's law, and (b) for a nonohmic device, in this case a semiconductor diode.

