

60 Hz (the unit “hertz,” as we saw in Chapter 11, means cycles per second). In many countries, 50 Hz is used.

Equation 18–2, $V = IR$, works also for ac: if a voltage V exists across a resistance R , then the current I through the resistance is

$$I = \frac{V}{R} = \frac{V_0}{R} \sin \omega t = I_0 \sin \omega t. \quad (18-7)$$

The quantity $I_0 = V_0/R$ is the **peak current**. The current is considered positive when the electrons flow in one direction and negative when they flow in the opposite direction. It is clear from Fig. 18–21b that an alternating current is as often positive as it is negative. Thus, the average current is zero. This does not mean, however, that no power is needed or that no heat is produced in a resistor. Electrons do move back and forth, and do produce heat. Indeed, the power transformed in a resistance R at any instant is

$$P = I^2 R = I_0^2 R \sin^2 \omega t.$$

Because the current is squared, we see that the power is always positive, as graphed in Fig. 18–22. The quantity $\sin^2 \omega t$ varies between 0 and 1; and it is not too difficult to show that its average value is $\frac{1}{2}$, as indicated in Fig. 18–22. Thus, the *average power* transformed, \bar{P} , is

$$\bar{P} = \frac{1}{2} I_0^2 R.$$

Since power can also be written $P = V^2/R = (V_0^2/R) \sin^2 \omega t$, we also have that the average power is

$$\bar{P} = \frac{1}{2} \frac{V_0^2}{R}.$$

The average or mean value of the *square* of the current or voltage is thus what is important for calculating average power: $\overline{I^2} = \frac{1}{2} I_0^2$ and $\overline{V^2} = \frac{1}{2} V_0^2$. The square root of each of these is the **rms** (root-mean-square) value of the current or voltage:

$$I_{\text{rms}} = \sqrt{\overline{I^2}} = \frac{I_0}{\sqrt{2}} = 0.707 I_0, \quad (18-8a) \quad \text{rms current}$$

$$V_{\text{rms}} = \sqrt{\overline{V^2}} = \frac{V_0}{\sqrt{2}} = 0.707 V_0. \quad (18-8b) \quad \text{rms voltage}$$

The rms values of V and I are sometimes called the *effective values*. They are useful because they can be substituted directly into the power formulas, Eqs. 18–5 and 18–6, to get the average power:

$$\bar{P} = I_{\text{rms}} V_{\text{rms}} \quad (18-9a)$$

$$\bar{P} = \frac{1}{2} I_0^2 R = I_{\text{rms}}^2 R \quad (18-9b)$$

$$\bar{P} = \frac{1}{2} \frac{V_0^2}{R} = \frac{V_{\text{rms}}^2}{R}. \quad (18-9c)$$

Thus, a direct current whose values of I and V equal the rms values of I and V for an alternating current will produce the same power. Hence it is usually the rms value of current that is specified or measured. For example, in the United States and Canada, standard line voltage[†] is 120-V ac. The 120 V is V_{rms} ; the peak voltage V_0 is

$$V_0 = \sqrt{2} V_{\text{rms}} = 170 \text{ V}.$$

In much of the world (Europe, Australia, Asia) the rms voltage is 240 V, so the peak voltage is 340 V.

[†]The line voltage can vary, depending on the total load; the frequency of 60 Hz or 50 Hz, however, remains extremely steady.

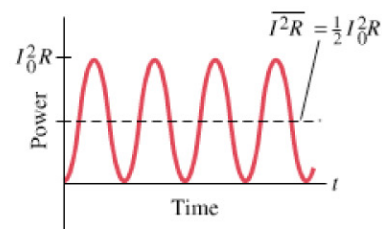


FIGURE 18–22 Power transformed in a resistor in an ac circuit.