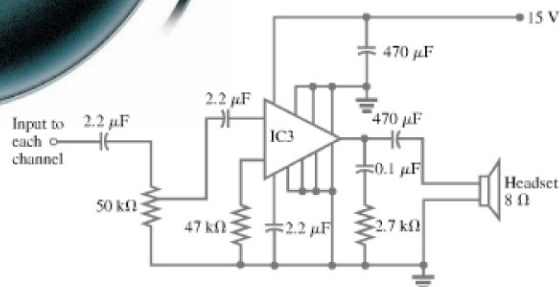


This portable MP3-CD player contains circuits that are dc, at least in part. (The audio signal is ac.) The circuit diagram below shows a possible amplifier circuit for each stereo channel. Although the large triangle is an amplifier chip containing transistors (discussed in Chapter 29), the other circuit elements are ones we have met, resistors and capacitors, and we discuss them in circuits in this Chapter. We also discuss voltmeters and ammeters, and how they are built and used to make measurements.



CHAPTER 19

DC Circuits

TABLE 19–1 Symbols for Circuit Elements

Symbol	Device
	Battery
	Capacitor
	Resistor
	Wire with negligible resistance
	Switch
	Ground

Electric circuits are basic parts of all electronic devices from radio and TV sets to computers and automobiles. Scientific measurements, from physics to biology and medicine, make use of electric circuits. In Chapter 18, we discussed the basic principles of electric current. Now we will apply these principles to analyze dc circuits involving combinations of batteries, resistors, and capacitors. We also study the operation of some useful instruments.[†]

When we draw a diagram for a circuit, we represent batteries, capacitors, and resistors by the symbols shown in Table 19–1. Wires whose resistance is negligible compared with other resistance in the circuit are drawn simply as straight lines. Some circuit diagrams show a ground symbol (or) which may mean a real connection to the ground, perhaps via a metal pipe, or it may simply mean a common connection, such as the frame of a car.

For the most part in this Chapter, except in Section 19–6 on RC circuits, we will be interested in circuits operating in their steady state. That is, we won't be looking at a circuit at the moment a change is made in it, such as when a battery or resistor is connected or disconnected, but rather a short time later when the currents have reached their steady values.

19–1 EMF and Terminal Voltage

To have current in an electric circuit, we need a device such as a battery or an electric generator that transforms one type of energy (chemical, mechanical, or light, for example) into electric energy. Such a device is called a **source of electromotive force** or of **emf**. (The term “electromotive force” is a misnomer since it does not refer to a “force” that is measured in newtons. Hence, to avoid confusion, we prefer to use the abbreviation, emf.) The *potential difference* between the terminals of such a source, when no current flows to an external circuit, is called the **emf** of the source. The symbol \mathcal{E} is usually used for emf (don't confuse it with E for electric field), and its unit is volts.

emf defined

[†]AC circuits that contain only a voltage source and resistors can be analyzed like the dc circuits in this Chapter. However, ac circuits that contain capacitors and other circuit elements are more complicated, and we discuss them in Chapter 21.