

A battery is not a source of constant current—the current out of a battery varies according to the resistance in the circuit. A battery *is*, however, a nearly constant voltage source, but not perfectly constant as we now discuss. You may have noticed in your own experience that when a current is drawn from a battery, the potential difference (voltage) across its terminals drops below its rated emf. For example, if you start a car with the headlights on, you may notice the headlights dim. This happens because the starter draws a large current, and the battery voltage drops as a result. The voltage drop occurs because the chemical reactions in a battery cannot supply charge fast enough to maintain the full emf. For one thing, charge must move (within the electrolyte) between the electrodes of the battery, and there is always some hindrance to completely free flow. Thus, a battery itself has some resistance, which is called its **internal resistance**; it is usually designated r .

A real battery is modeled as if it were a perfect emf \mathcal{E} in series with a resistor r , as shown in Fig. 19–1. Since this resistance r is inside the battery, we can never separate it from the battery. The two points a and b in the diagram represent the two terminals of the battery. What we measure is the **terminal voltage** $V_{ab} = V_a - V_b$. When no current is drawn from the battery, the terminal voltage equals the emf, which is determined by the chemical reactions in the battery: $V_{ab} = \mathcal{E}$. However, when a current I flows naturally from the battery there is an internal drop in voltage equal to Ir . Thus the terminal voltage (the actual voltage) is[†]

$$V_{ab} = \mathcal{E} - Ir. \quad (19-1)$$

For example, if a 12-V battery has an internal resistance of 0.1Ω , then when 10 A flows from the battery, the terminal voltage is $12 \text{ V} - (10 \text{ A})(0.1 \Omega) = 11 \text{ V}$. The internal resistance of a battery is usually small. For example, an ordinary flashlight battery when fresh may have an internal resistance of perhaps 0.05Ω . (However, as it ages and the electrolyte dries out, the internal resistance increases to many ohms.) Car batteries have lower internal resistance.

EXAMPLE 19–1 Battery with internal resistance. A $65.0\text{-}\Omega$ resistor is connected to the terminals of a battery whose emf is 12.0 V and whose internal resistance is 0.5Ω , Fig. 19–2. Calculate (a) the current in the circuit, (b) the terminal voltage of the battery, V_{ab} , and (c) the power dissipated in the resistor R and in the battery's internal resistance r .

APPROACH We first consider the battery as a whole, which is shown in Fig. 19–2 as an emf \mathcal{E} and internal resistance r between points a and b . Then we apply $V = IR$ to the circuit itself.

SOLUTION (a) From Eq. 19–1, we have

$$V_{ab} = \mathcal{E} - Ir.$$

We apply Ohm's law (Eq. 18–2) to this battery and the resistance R of the circuit: $V_{ab} = IR$. Hence $IR = \mathcal{E} - Ir$ or $\mathcal{E} = I(R + r)$, and so

$$I = \frac{\mathcal{E}}{R + r} = \frac{12.0 \text{ V}}{65.0 \Omega + 0.5 \Omega} = \frac{12.0 \text{ V}}{65.5 \Omega} = 0.183 \text{ A}.$$

(b) The terminal voltage is

$$V_{ab} = \mathcal{E} - Ir = 12.0 \text{ V} - (0.183 \text{ A})(0.5 \Omega) = 11.9 \text{ V}.$$

(c) The power dissipated (Eq. 18–6) in R is

$$P_R = I^2 R = (0.183 \text{ A})^2 (65.0 \Omega) = 2.18 \text{ W},$$

and in r is

$$P_r = I^2 r = (0.183 \text{ A})^2 (0.5 \Omega) = 0.02 \text{ W}.$$

EXERCISE A Repeat Example 19–1 assuming now that the resistance $R = 10.0 \Omega$, whereas \mathcal{E} and r remain as before.

[†]When a battery is being charged, a current is forced to pass through it; we then have to write

$$V_{ab} = \mathcal{E} + Ir.$$

See Example 19–9 or Problem 24 and Fig. 19–44.

CAUTION

Why battery voltage isn't perfectly constant

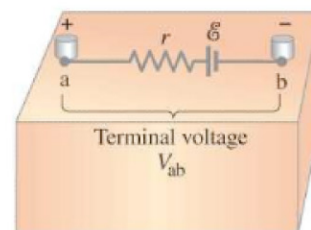


FIGURE 19–1 Diagram for an electric cell or battery.

Terminal voltage

FIGURE 19–2 Example 19–1.

