

**FIGURE 19-5** Water pipes in parallel—analogy to electric currents in parallel.

The equivalent resistance of the two  $4\text{-}\Omega$  “resistors” in parallel is

$$\frac{1}{R_{\text{eq}}} = \frac{1}{4\ \Omega} + \frac{1}{4\ \Omega} = \frac{2}{4\ \Omega} = \frac{1}{2\ \Omega},$$


and so  $R_{\text{eq}} = 2\ \Omega$ . Thus the net (or equivalent) resistance is *less* than each single resistance. This may at first seem surprising. But remember that when you connect resistors in parallel, you are giving the current additional paths to follow. Hence the net resistance will be less.

An analogy may help here. Consider two identical pipes taking in water near the top of a dam and releasing it below as shown in Fig. 19-5. The gravitational potential difference, proportional to the height  $h$ , is the same for both pipes, just as the voltage is the same for parallel resistors. If both pipes are open, rather than only one, twice as much water will flow through. That is, with two equal pipes open, the net resistance to the flow of water will be reduced, by half, just as for electrical resistors in parallel. Note that if both pipes are closed, the dam offers infinite resistance to the flow of water. This corresponds in the electrical case to an open circuit—when the path is not continuous and no current flows—so the electrical resistance is infinite.

**CONCEPTUAL EXAMPLE 19-2** **Series or parallel?** (a) The lightbulbs in Fig. 19-6 are identical and have identical resistance  $R$ . Which configuration produces more light? (b) Which way do you think the headlights of a car are wired?

**RESPONSE** (a) The equivalent resistance of the parallel circuit is found from Eq. 19-4,  $1/R_{\text{eq}} = 1/R + 1/R = 2/R$ . Thus  $R_{\text{eq}} = R/2$ . The parallel combination then has lower resistance ( $= R/2$ ) than the series combination ( $R_{\text{eq}} = R + R = 2R$ ). There will be more total current in the parallel configuration (2), since  $I = V/R_{\text{eq}}$  and  $V$  is the same for both circuits. The total power transformed, which is related to the light produced, is  $P = IV$ , so the greater current in (2) means more light produced.

(b) Headlights are wired in parallel (2), because if one bulb goes out, the other bulb can stay lit. If they were in series (1), when one bulb burned out (the filament broke), the circuit would be open and no current would flow, so even the good bulb would not light.

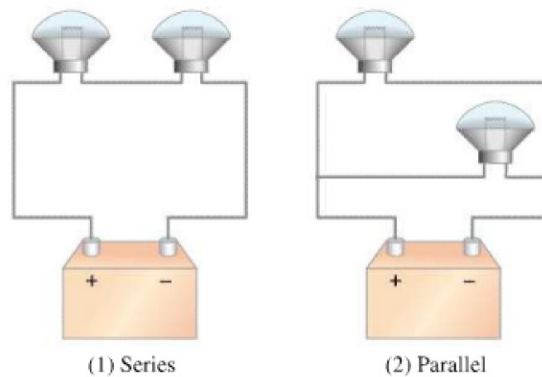

**FIGURE 19-6** Example 19-2.

**EXAMPLE 19-3** **Series and parallel resistors.** Two  $100\text{-}\Omega$  resistors are connected (a) in parallel, and (b) in series, to a  $24.0\text{-V}$  battery. See Fig. 19-7. What is the current through each resistor and what is the equivalent resistance of each circuit?

**APPROACH** We use Ohm’s law and the ideas just discussed for series and parallel connections to get the current in each case. We can also use Eqs. 19-3 and 19-4.