
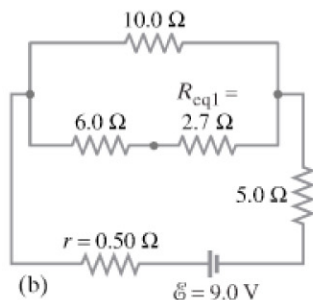



(a)

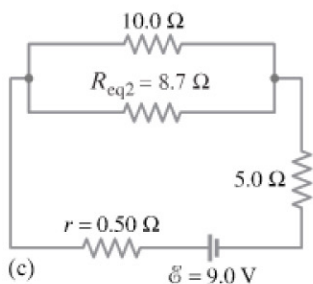

(b)




(c)

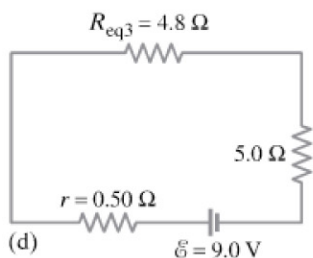

(d)

**FIGURE 19-10** Circuit for Example 19-7, where  $r$  is the internal resistance of the battery.

**FIGURE 19-11** Currents can be calculated using Kirchhoff's rules.

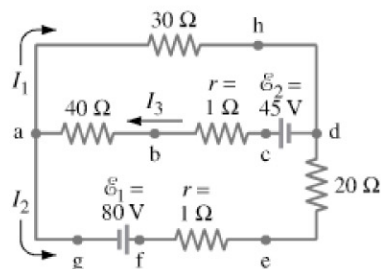

### Additional Example

**EXAMPLE 19-7 Analyzing a circuit.** A 9.0-V battery whose internal resistance  $r$  is  $0.50\ \Omega$  is connected in the circuit shown in Fig. 19-10a. (a) How much current is drawn from the battery? (b) What is the terminal voltage of the battery? (c) What is the current in the  $6.0\text{-}\Omega$  resistor?

**APPROACH** To find the current out of the battery, we first need to determine the equivalent resistance  $R_{\text{eq}}$  of the entire circuit, including  $r$ , which we do by identifying and isolating simple series or parallel combinations of resistors. Once we find  $I$  from Ohm's law,  $I = \mathcal{E}/R_{\text{eq}}$ , we get the terminal voltage using  $V_{\text{ab}} = \mathcal{E} - Ir$ . For (c) we apply Ohm's law to the  $6.0\text{-}\Omega$  resistor.

**SOLUTION** (a) We want to determine the equivalent resistance of the circuit. But where do we start? We note that the  $4.0\text{-}\Omega$  and  $8.0\text{-}\Omega$  resistors are in parallel, and so have an equivalent resistance  $R_{\text{eq1}}$  given by

$$\frac{1}{R_{\text{eq1}}} = \frac{1}{8.0\ \Omega} + \frac{1}{4.0\ \Omega} = \frac{3}{8.0\ \Omega};$$

so  $R_{\text{eq1}} = 2.7\ \Omega$ . This  $2.7\ \Omega$  is in series with the  $6.0\text{-}\Omega$  resistor, as shown in the equivalent circuit of Fig. 19-10b. The net resistance of the lower arm of the circuit is then

$$R_{\text{eq2}} = 6.0\ \Omega + 2.7\ \Omega = 8.7\ \Omega,$$

as shown in Fig. 19-10c. The equivalent resistance  $R_{\text{eq3}}$  of the  $8.7\text{-}\Omega$  and  $10.0\text{-}\Omega$  resistances in parallel is given by

$$\frac{1}{R_{\text{eq3}}} = \frac{1}{10.0\ \Omega} + \frac{1}{8.7\ \Omega} = 0.21\ \Omega^{-1},$$

so  $R_{\text{eq3}} = (1/0.21\ \Omega^{-1}) = 4.8\ \Omega$ . This  $4.8\ \Omega$  is in series with the  $5.0\text{-}\Omega$  resistor and the  $0.50\text{-}\Omega$  internal resistance of the battery (Fig. 19-10d), so the total equivalent resistance  $R_{\text{eq}}$  of the circuit is  $R_{\text{eq}} = 4.8\ \Omega + 5.0\ \Omega + 0.50\ \Omega = 10.3\ \Omega$ . Hence the current drawn is

$$I = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{9.0\ \text{V}}{10.3\ \Omega} = 0.87\ \text{A}.$$

(b) The terminal voltage of the battery is

$$V_{\text{ab}} = \mathcal{E} - Ir = 9.0\ \text{V} - (0.87\ \text{A})(0.50\ \Omega) = 8.6\ \text{V}.$$

(c) Now we can work back and get the current in the  $6.0\text{-}\Omega$  resistor. It must be the same as the current through the  $8.7\ \Omega$  shown in Fig. 19-10c (why?). The voltage across that  $8.7\ \Omega$  will be the emf of the battery minus the voltage drops across  $r$  and the  $5.0\text{-}\Omega$  resistor:  $V_{8.7} = 9.0\ \text{V} - (0.87\ \text{A})(0.50\ \Omega + 5.0\ \Omega)$ . Applying Ohm's law, we get the current (call it  $I'$ )

$$I' = \frac{9.0\ \text{V} - (0.87\ \text{A})(0.50\ \Omega + 5.0\ \Omega)}{8.7\ \Omega} = 0.48\ \text{A}.$$

This is the current through the  $6.0\text{-}\Omega$  resistor.

## 19-3 Kirchhoff's Rules

In the last few Examples we have been able to find the currents in circuits by combining resistances in series and parallel, and using Ohm's law. This technique can be used for many circuits. However, some circuits are too complicated for that analysis. For example, we cannot find the currents in each part of the circuit shown in Fig. 19-11 simply by combining resistances as we did before.

To deal with such complicated circuits, we use Kirchhoff's rules, devised by G. R. Kirchhoff (1824–1887) in the mid-nineteenth century. There are two rules, and they are simply convenient applications of the laws of conservation of charge and