

4. Loop rule: We apply Kirchhoff's loop rule to two different closed loops. First we apply it to the upper loop ahdcba. We start (and end) at point a. From a to h we have a potential decrease $V_{ha} = -(I_1)(30\ \Omega)$. From h to d there is no change, but from d to c the potential increases by 45 V: that is, $V_{cd} = +45\ \text{V}$. From c to a the potential decreases through the two resistances by an amount $V_{ac} = -(I_3)(40\ \Omega + 1\ \Omega) = -(41\ \Omega)I_3$. Thus we have $V_{ha} + V_{cd} + V_{ac} = 0$, or

$$-30I_1 + 45 - 41I_3 = 0, \quad (b)$$

where we have omitted the units. For our second loop, we take the outer loop ahdefga. (We could have chosen the lower loop abcdefga instead.) Again we start at point a and have $V_{ha} = -(I_1)(30\ \Omega)$, and $V_{dh} = 0$. But when we take our positive test charge from d to e, it actually is going uphill, against the current—or at least against the *assumed* direction of the current, which is what counts in this calculation. Thus $V_{ed} = I_2(20\ \Omega)$ has a *positive* sign. Similarly, $V_{fe} = I_2(1\ \Omega)$. From f to g there is a decrease in potential of 80 V since we go from the high potential terminal of the battery to the low. Thus $V_{gf} = -80\ \text{V}$. Finally, $V_{ag} = 0$, and the sum of the potential changes around this loop is then

$$-30I_1 + (20 + 1)I_2 - 80 = 0. \quad (c)$$

5. Solve the equations. We have three equations—labeled (a), (b), and (c)—and three unknowns. From Eq. (c) we have

$$I_2 = \frac{80 + 30I_1}{21} = 3.8 + 1.4I_1. \quad (d)$$

From Eq. (b) we have

$$I_3 = \frac{45 - 30I_1}{41} = 1.1 - 0.73I_1. \quad (e)$$

We substitute Eqs. (d) and (e) into Eq. (a):

$$I_1 = I_3 - I_2 = 1.1 - 0.73I_1 - 3.8 - 1.4I_1.$$

We solve for I_1 , collecting terms:

$$3.1I_1 = -2.7$$

$$I_1 = -0.87\ \text{A}.$$

The negative sign indicates that the direction of I_1 is actually opposite to that initially assumed and shown in Fig. 19–13. Note that the answer automatically comes out in amperes because all values were in volts and ohms. From Eq. (d) we have

$$I_2 = 3.8 + 1.4I_1 = 3.8 + 1.4(-0.87) = 2.6\ \text{A},$$

and from Eq. (e)

$$I_3 = 1.1 - 0.73I_1 = 1.1 - 0.73(-0.87) = 1.7\ \text{A}.$$

This completes the solution.

NOTE The unknowns in different situations are not necessarily currents. It might be that the currents are given and we have to solve for unknown resistance or voltage.

EXERCISE C Write the equation for the lower loop abcdefga of Example 19–8 and show, assuming the currents calculated in this Example, that the potentials add to zero for this lower loop.