

SOLUTION (a) The circuit with only the weak battery and no jumper cables is simple: an emf of 10.1 V connected to two resistances in series, $0.10\ \Omega + 0.15\ \Omega = 0.25\ \Omega$. Hence the current is $I = V/R = (10.1\ \text{V})/(0.25\ \Omega) = 40\ \text{A}$.

(b) We need to find the resistance of the jumper cables that connect the good battery. From Eq. 18-3, each has resistance $R_J = \rho L/A = (1.68 \times 10^{-8}\ \Omega \cdot \text{m})(3.0\ \text{m})/(\pi)(0.25 \times 10^{-2}\ \text{m})^2 = 0.0026\ \Omega$. Kirchhoff's loop rule for the full outside loop gives

$$\begin{aligned} 12.5\ \text{V} - I_1(2R_J + r_1) - I_3 R_S &= 0 \\ 12.5\ \text{V} - I_1(0.025\ \Omega) - I_3(0.15\ \Omega) &= 0 \end{aligned} \quad (a)$$

since $(2R_J + r) = (0.0052\ \Omega + 0.020\ \Omega) = 0.025\ \Omega$.

The loop rule for the lower loop, including the weak battery and the starter, gives

$$10.1\ \text{V} - I_3(0.15\ \Omega) - I_2(0.10\ \Omega) = 0. \quad (b)$$

The junction rule at point B gives

$$I_1 + I_2 = I_3. \quad (c)$$

We have three equations in three unknowns. From Eq. (c), $I_1 = I_3 - I_2$ and we substitute this into Eq. (a):

$$\begin{aligned} 12.5\ \text{V} - (I_3 - I_2)(0.025\ \Omega) - I_3(0.15\ \Omega) &= 0, \\ 12.5\ \text{V} - I_3(0.175\ \Omega) + I_2(0.025\ \Omega) &= 0. \end{aligned}$$

Combining this last equation with (b) gives $I_3 = 71\ \text{A}$, quite a bit better than in (a). The other currents are $I_2 = -5\ \text{A}$ and $I_1 = 76\ \text{A}$. Note that $I_2 = -5\ \text{A}$ is in the opposite direction from that assumed in Fig. 19-15. The terminal voltage of the weak 10.1-V battery is thus $V_{BA} = 10.1\ \text{V} - (-5\ \text{A})(0.10\ \Omega) = 10.6\ \text{V}$.

NOTE The circuit shown in Fig. 19-15, without the starter motor, is how a battery can be charged. The stronger battery pushes charge back into the weaker battery.

EXERCISE D If the jumper cables of Example 19-9 were mistakenly connected in reverse, the positive terminal of each battery would be connected to the negative terminal of the other battery (Fig. 19-16). What would be the current I even before the starter motor is engaged (the switch S in Fig. 19-16 is open)? Why could this cause the batteries to explode?

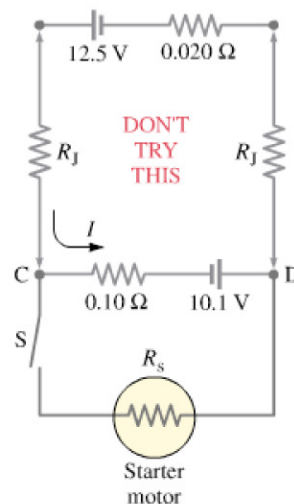


FIGURE 19-16 Exercise D.

19-5 Circuits Containing Capacitors in Series and in Parallel

Just as resistors can be placed in series or in parallel in a circuit, so can capacitors (Chapter 17). We first consider a **parallel** connection as shown in Fig. 19-17. If a battery supplies a potential difference V to points a and b , this same potential difference $V = V_{ab}$ exists across each of the capacitors. That is, since the left-hand plates of all the capacitors are connected by conductors, they all reach the same potential V_a when connected to the battery; and the right-hand plates each reach potential V_b . Each capacitor plate acquires a charge given by $Q_1 = C_1 V$, $Q_2 = C_2 V$, and $Q_3 = C_3 V$. The total charge Q that must leave the battery is then

$$Q = Q_1 + Q_2 + Q_3 = C_1 V + C_2 V + C_3 V.$$

Let us try to find a single equivalent capacitor that will hold the same charge Q at the same voltage $V = V_{ab}$. It will have a capacitance C_{eq} given by

$$Q = C_{eq} V.$$

Combining the two previous equations, we have

$$C_{eq} V = C_1 V + C_2 V + C_3 V = (C_1 + C_2 + C_3) V$$

or

$$C_{eq} = C_1 + C_2 + C_3. \quad [\text{parallel}] \quad (19-5) \quad \text{Capacitors in parallel}$$

The net effect of connecting capacitors in parallel is thus to *increase* the capacitance. This makes sense because we are essentially increasing the area of the plates where charge can accumulate (see, for example, Eq. 17-8).

FIGURE 19-17 Capacitors in parallel: $C_{eq} = C_1 + C_2 + C_3$.

