

### \* Additional Example—Calculating Charge and Voltage

**EXAMPLE 19–11 Charge and voltage on capacitors.** Determine the charge on each capacitor in Fig. 19–19a of Example 19–10, and the voltage across each, assuming  $C = 3.0 \mu\text{F}$  and the battery voltage is  $V = 4.0 \text{ V}$ .

**APPROACH** We have to work “backward” through Example 19–10. That is, we find the charge  $Q$  that leaves the battery, using the equivalent capacitance. Then we find the charge on each separate capacitor and the voltage across each. Each step uses Eq. 17–7,  $Q = CV$ .

**SOLUTION** The 4.0-V battery “thinks” it is connected to a capacitance  $C_{\text{eq}} = \frac{2}{3}C = \frac{2}{3}(3.0 \mu\text{F}) = 2.0 \mu\text{F}$ . Therefore the charge  $Q$  that leaves the battery, by Eq. 17–7, is

$$Q = CV = (2.0 \mu\text{F})(4.0 \text{ V}) = 8.0 \mu\text{C}.$$

From Fig. 19–19a, this charge arrives at the negative plate of  $C_1$ , so  $Q_1 = 8.0 \mu\text{C}$ . The charge  $Q$  that leaves the positive plate is split evenly between  $C_2$  and  $C_3$  (symmetry:  $C_2 = C_3$ ) and is  $Q_2 = Q_3 = \frac{1}{2}Q = 4.0 \mu\text{C}$ . Also, the voltages across  $C_2$  and  $C_3$  have to be the same. The voltage across each capacitor is obtained using  $V = Q/C$ . So

$$V_1 = Q_1/C_1 = (8.0 \mu\text{C})/(3.0 \mu\text{F}) = 2.7 \text{ V}$$


$$V_2 = Q_2/C_2 = (4.0 \mu\text{C})/(3.0 \mu\text{F}) = 1.3 \text{ V}$$

$$V_3 = Q_3/C_3 = (4.0 \mu\text{C})/(3.0 \mu\text{F}) = 1.3 \text{ V}.$$

## 19–6 RC Circuits—Resistor and Capacitor in Series

Capacitors and resistors are often found together in a circuit. Such **RC circuits** are used to control a car’s windshield wipers and the timing of traffic lights; they are used in camera flashes, in heart pacemakers, and many other electronic devices. In **RC circuits**, we are not so interested in the final “steady state” voltage and charge on the capacitor, but rather in how these variables change in time. A simple example is shown in Fig. 19–20a. We now analyze this **RC circuit**.

*RC circuits*

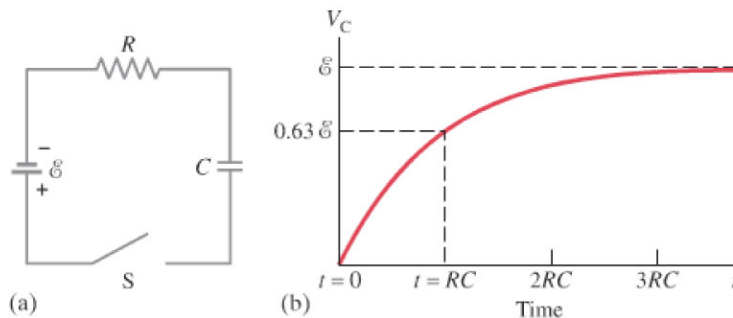

**FIGURE 19–20** For the **RC circuit** shown in (a), the voltage across the capacitor increases with time, as shown in (b), after the switch **S** is closed.

When the switch **S** is closed, current immediately begins to flow through the circuit. Electrons will flow out from the negative terminal of the battery, through the resistor **R**, and accumulate on the upper plate of the capacitor. And electrons will flow into the positive terminal of the battery, leaving a positive charge on the other plate of the capacitor. As charge accumulates on the capacitor, the potential difference across it increases ( $V = Q/C$ ), and the current is reduced until eventually the voltage across the capacitor equals the emf of the battery,  $\mathcal{E}$ . There is then no potential difference across the resistor, and no further current flow. The potential difference across the capacitor, which is proportional to the charge on the capacitor ( $V_C = Q/C$ , Eq. 17–7), thus increases in time, as shown in Fig. 19–20b. The actual shape of this curve is a type of exponential. It is given by the formula<sup>†</sup>

*Charging the capacitor*

$$V_C = \mathcal{E}(1 - e^{-t/RC}),$$

where we use the subscript **c** to remind us that  $V_C$  is the voltage across the capacitor and is given here as a function of time  $t$ . [The constant  $e$ , known as the base for natural logarithms, has the value  $e = 2.718\cdots$ . Do not confuse this  $e$  with  $e$  for the charge on the electron.]

**⚠ CAUTION**  
Don't confuse  $e$  for exponential with  $e$  for electron charge

<sup>†</sup>The derivation uses calculus.