

We can write a similar formula for the charge $Q (= CV_C)$ on the capacitor:

$$Q = Q_0(1 - e^{-t/RC}),$$

where Q_0 represents the maximum charge.

The product of the resistance R times the capacitance C , which appears in the exponent, is called the **time constant** τ of the circuit:

$$\text{Time constant } \tau = RC \qquad \tau = RC. \qquad (19-7)$$

The time constant is a measure of how quickly the capacitor becomes charged. [The units of RC are $\Omega \cdot \text{F} = (\text{V}/\text{A})(\text{C}/\text{V}) = \text{C}/(\text{C}/\text{s}) = \text{s}$.] Specifically, it can be shown that the product RC gives the time required for the capacitor's voltage (and charge) to reach 63% of the maximum. This can be checked[†] using any calculator with an e^x key: $e^{-1} = 0.37$, so for $t = RC$, then $(1 - e^{-t/RC}) = (1 - e^{-1}) = (1 - 0.37) = 0.63$. In a circuit, for example, where $R = 200 \text{ k}\Omega$ and $C = 3.0 \mu\text{F}$, the time constant is $(2.0 \times 10^5 \Omega)(3.0 \times 10^{-6} \text{ F}) = 0.60 \text{ s}$. If the resistance is much smaller, the time constant is much smaller and the capacitor becomes charged almost instantly. This makes sense, since a lower resistance will retard the flow of charge less. All circuits contain some resistance (if only in the connecting wires), so a capacitor can never be charged instantaneously when connected to a battery.

Capacitor discharges

The circuit just discussed involved the *charging* of a capacitor by a battery through a resistance. Now let us look at another situation: a capacitor is already charged (say, to a voltage V_0 and charge Q_0), and it is then allowed to *discharge* through a resistance R as shown in Fig. 19-21a. (In this case there is no battery.) When the switch S is closed, charge begins to flow through resistor R from one side of the capacitor toward the other side, until it is fully discharged. The voltage across the capacitor decreases, as shown in Fig. 19-21b. This "exponential decay" curve is given by


$$V_C = V_0 e^{-t/RC},$$

where V_0 is the initial voltage across the capacitor. The voltage falls 63% of the way to zero (to $0.37V_0$) in a time $\tau = RC$. Because the charge Q on the capacitor is $Q = CV$, we can write

$$Q = Q_0 e^{-t/RC}$$

for a discharging capacitor, where Q_0 is the initial charge.

FIGURE 19-21 For the RC circuit shown in (a), the voltage V_C on the capacitor decreases with time, as shown in (b), after the switch S is closed. The charge on the capacitor follows the same curve since $Q \propto V$.

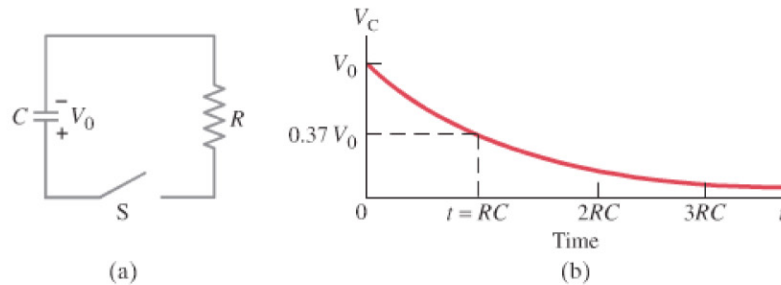

EXAMPLE 19-12 A discharging RC circuit. If a charged capacitor, $C = 35 \mu\text{F}$, is connected to a resistance $R = 120 \Omega$ as in Fig. 19-21a, how much time will elapse until the voltage falls to 10% of its original (maximum) value?

APPROACH The voltage across the capacitor decreases according to $V_C = V_0 e^{-t/RC}$. We set $V_C = 0.10V_0$ (10% of V_0), but first we need to calculate $\tau = RC$.

[†]More simply, since $e = 2.718\dots$, then $e^{-1} = 1/e = 1/2.718 = 0.37$. Note that e is the inverse operation to the natural logarithm \ln : $\ln(e) = 1$, and $\ln(e^x) = x$.