

Like an inductor, the voltage and current are out of phase by 90° . But for a capacitor, the current reaches its peaks $\frac{1}{4}$ cycle before the voltage does, so we say that the

current leads the voltage by 90° in a capacitor.

Because the current and voltage are out of phase, the average power dissipated is zero, just as for an inductor. Thus *only a resistance will dissipate energy* as thermal energy in an ac circuit.

A relationship between the applied voltage and the current in a capacitor can be written just as for an inductance:

$$V = IX_C, \quad \left[\begin{array}{l} \text{rms or peak} \\ \text{values} \end{array} \right] \quad (21-12a)$$

where X_C is the **capacitive reactance** and has units of ohms. V and I can both be rms or both maximum (V_0 and I_0); X_C depends on both the capacitance C and the frequency f :

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}, \quad (21-12b) \quad \text{Capacitive reactance}$$

where $\omega = 2\pi f$. For dc conditions, $f = 0$ and X_C becomes infinite, as it should because a capacitor does not pass dc current.

EXAMPLE 21-17 Capacitor reactance. What is the rms current in the circuit of Fig. 21-37a if $C = 1.0 \mu\text{F}$ and $V_{\text{rms}} = 120 \text{ V}$? Calculate for (a) $f = 60 \text{ Hz}$, and then for (b) $f = 6.0 \times 10^5 \text{ Hz}$.

APPROACH We find the reactance using Eq. 21-12b, and solve for current in the equivalent form of Ohm's law, Eq. 21-12a.

SOLUTION (a) $X_C = 1/2\pi f C = 1/(6.28)(60 \text{ s}^{-1})(1.0 \times 10^{-6} \text{ F}) = 2.7 \text{ k}\Omega$.

The rms current is (Eq. 21-12a):

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_C} = \frac{120 \text{ V}}{2.7 \times 10^3 \Omega} = 44 \text{ mA}.$$

(b) For $f = 6.0 \times 10^5 \text{ Hz}$, X_C will be 0.27Ω and $I_{\text{rms}} = 440 \text{ A}$, vastly larger!

NOTE The dependence on f is dramatic. For high frequencies, the capacitive reactance is very small.

Two common applications of capacitors are illustrated in Fig. 21-38a and b. In Fig. 21-38a, circuit A is said to be capacitively coupled to circuit B. The purpose of the capacitor is to prevent a dc voltage from passing from A to B but allowing an ac signal to pass relatively unimpeded (if C is sufficiently large). In Fig. 21-38b, the

Capacitor: current leads voltage

Only R (not C or L) dissipates energy

PHYSICS APPLIED
Capacitors as filters

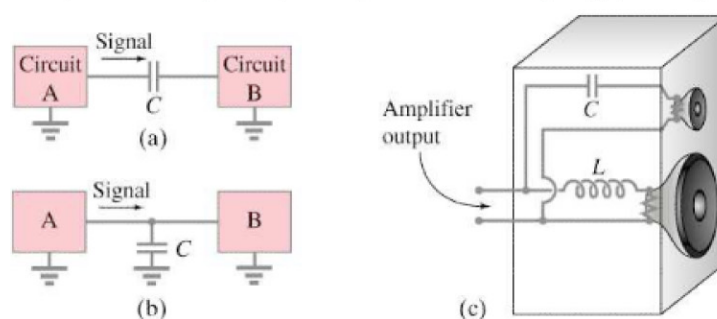


FIGURE 21-38 (a) (b) Two common uses for a capacitor. (c) Simple loudspeaker cross-over.

capacitor also passes ac but not dc. In this case, a dc voltage can be maintained between circuits A and B, but an ac signal leaving A passes to ground instead of into B. Thus the capacitor in Fig. 21-38b acts like a *filter* when a constant dc voltage is required; any sharp variation in voltage will pass to ground instead of into circuit B.

Loudspeakers having separate “woofer” (low-frequency speaker) and “tweeter” (high-frequency speaker) may use a simple “cross-over” that consists of a capacitor in the tweeter circuit to impede low-frequency signals, and an inductor in the woofer circuit to impede high-frequency signals ($X_L = 2\pi f L$). Hence mainly low-frequency sounds reach and are emitted by the woofer. See Fig. 21-38c.

PHYSICS APPLIED
Loudspeaker cross-over