

FIGURE 29-28 Current through a diode as a function of applied voltage.

EXAMPLE 29-6 **A diode.** The diode whose current–voltage characteristics are shown in Fig. 29-28 is connected in series with a 4.0-V battery and a resistor. If a current of 15 mA is to pass through the diode, what resistance must the resistor have?

APPROACH We use Fig. 29-28, where we see that the voltage drop across the diode is about 0.7 V when the current is 15 mA. Then we use simple circuit analysis and Ohm’s law (Chapters 18 and 19).

SOLUTION The voltage drop across the resistor is $4.0\text{ V} - 0.7\text{ V} = 3.3\text{ V}$, so $R = V/I = (3.3\text{ V})/(1.5 \times 10^{-2}\text{ A}) = 220\ \Omega$.

The symbol for a diode is



[diode]

where the arrow represents the direction conventional (+) current flows readily.

Since a *pn* junction diode allows current to flow only in one direction (as long as the voltage is not too high), it can serve as a **rectifier**—to change ac into dc. A simple rectifier circuit is shown in Fig. 29-29a. The ac source applies a voltage across the diode alternately positive and negative. Only during half of each cycle will a current pass through the diode; only then is there a current through the resistor R . Hence, a graph of the voltage V_{ab} across R as a function of time looks like the output voltage shown in Fig. 29-29b. This **half-wave rectification** is not exactly dc, but it is unidirectional. More useful is a **full-wave rectifier** circuit, which uses two diodes (or sometimes four) as shown in Fig. 29-30a. At any given instant, either one diode or the other will conduct current to the right. Therefore, the output across the load resistor R will be as shown in Fig. 29-30b. Actually this is the voltage if the capacitor C were not in the circuit. The capacitor tends to store charge and, if the time constant RC is sufficiently long, helps to smooth out the current as shown in Fig. 29-30c. (The variation in output shown in Fig. 29-30c is called *ripple voltage*.)

Rectifier circuits are important because most line voltage in buildings is ac, and most electronic devices require a dc voltage for their operation. Hence, diodes are found in nearly all electronic devices including radio and TV sets, calculators, and computers.

FIGURE 29-29 (a) A simple (half-wave) rectifier circuit using a semiconductor diode. (b) AC source input voltage, and output voltage across R , as functions of time.

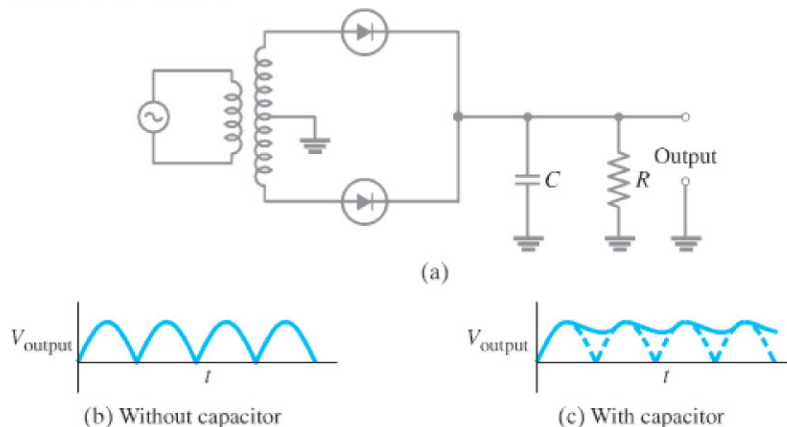
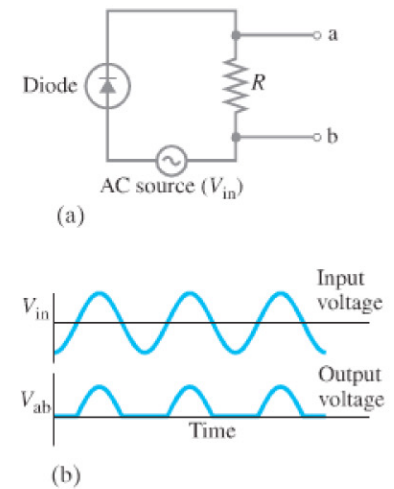


FIGURE 29-30 (a) Full-wave-rectifier circuit (including a transformer so the magnitude of the voltage can be changed). (b) Output voltage in the absence of capacitor C . (c) Output voltage with the capacitor in the circuit.