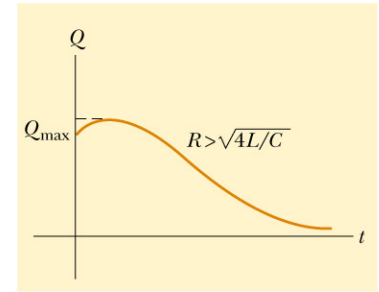


**Figure 32.21** (a) Charge versus time for a damped  $RLC$  circuit. The charge decays in this way when  $R \ll \sqrt{4L/C}$ . The  $Q$ -versus- $t$  curve represents a plot of Equation 32.31. (b) Oscilloscope pattern showing the decay in the oscillations of an  $RLC$  circuit. The parameters used were  $R = 75 \Omega$ ,  $L = 10 \text{ mH}$ , and  $C = 0.19 \mu\text{F}$ .



**Figure 32.22** Plot of  $Q$  versus  $t$  for an overdamped  $RLC$  circuit, which occurs for values of  $R > \sqrt{4L/C}$ .

## SUMMARY

When the current in a coil changes with time, an emf is induced in the coil according to Faraday's law. The **self-induced emf** is

$$\mathcal{E}_L = -L \frac{dI}{dt} \quad (32.1)$$

where  $L$  is the **inductance** of the coil. Inductance is a measure of how much opposition an electrical device offers to a change in current passing through the device. Inductance has the SI unit of **henry** (H), where  $1 \text{ H} = 1 \text{ V} \cdot \text{s}/\text{A}$ .

The inductance of any coil is

$$L = \frac{N\Phi_B}{I} \quad (32.2)$$

where  $\Phi_B$  is the magnetic flux through the coil and  $N$  is the total number of turns. The inductance of a device depends on its geometry. For example, the inductance of an air-core solenoid is

$$L = \frac{\mu_0 N^2 A}{\ell} \quad (32.4)$$

where  $A$  is the cross-sectional area, and  $\ell$  is the length of the solenoid.

If a resistor and inductor are connected in series to a battery of emf  $\mathcal{E}$ , and if a switch in the circuit is thrown closed at  $t = 0$ , then the current in the circuit varies in time according to the expression

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \quad (32.7)$$

where  $\tau = L/R$  is the time constant of the  $RL$  circuit. That is, the current increases to an equilibrium value of  $\mathcal{E}/R$  after a time that is long compared with  $\tau$ . If the battery in the circuit is replaced by a resistanceless wire, the current decays exponentially with time according to the expression

$$I = \frac{\mathcal{E}}{R} e^{-t/\tau} \quad (32.10)$$

where  $\mathcal{E}/R$  is the initial current in the circuit.