

The **impedance**  $Z$  of an  $RLC$  series ac circuit, which also has the ohm as its unit, is

$$Z \equiv \sqrt{R^2 + (X_L - X_C)^2} \quad (33.23)$$

This expression illustrates that we cannot simply add the resistance and reactances in a circuit. We must account for the fact that the applied voltage and current are out of phase, with the **phase angle**  $\phi$  between the current and voltage being

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) \quad (33.25)$$

The sign of  $\phi$  can be positive or negative, depending on whether  $X_L$  is greater or less than  $X_C$ . The phase angle is zero when  $X_L = X_C$ .

The **average power** delivered by the generator in an  $RLC$  ac circuit is

$$\mathcal{P}_{\text{av}} = I_{\text{rms}} \Delta V_{\text{rms}} \cos \phi \quad (33.29)$$

An equivalent expression for the average power is

$$\mathcal{P}_{\text{av}} = I_{\text{rms}}^2 R \quad (33.30)$$

The average power delivered by the generator results in increasing internal energy in the resistor. No power loss occurs in an ideal inductor or capacitor.

The rms current in a series  $RLC$  circuit is

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{\sqrt{R^2 + (X_L - X_C)^2}} \quad (33.32)$$

A series  $RLC$  circuit is in resonance when the inductive reactance equals the capacitive reactance. When this condition is met, the current given by Equation 33.32 reaches its maximum value. When  $X_L = X_C$  in a circuit, the **resonance frequency**  $\omega_0$  of the circuit is

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (33.33)$$

The current in a series  $RLC$  circuit reaches its maximum value when the frequency of the generator equals  $\omega_0$ —that is, when the “driving” frequency matches the resonance frequency.

Transformers allow for easy changes in alternating voltage. Because energy (and therefore power) are conserved, we can write

$$I_1 \Delta V_1 = I_2 \Delta V_2 \quad (33.40)$$

to relate the currents and voltages in the primary and secondary windings of a transformer.

## QUESTIONS

- Fluorescent lights flicker on and off 120 times every second. Explain what causes this. Why can't you see it happening?
- Why does a capacitor act as a short circuit at high frequencies? Why does it act as an open circuit at low frequencies?
- Explain how the acronyms in the mnemonic “ELI the ICE man” can be used to recall whether current leads voltage or voltage leads current in  $RLC$  circuits. (Note that “E” represents voltage.)
- Why is the sum of the maximum voltages across the elements in a series  $RLC$  circuit usually greater than the maximum applied voltage? Doesn't this violate Kirchhoff's second rule?
- Does the phase angle depend on frequency? What is the phase angle when the inductive reactance equals the capacitive reactance?
- Energy is delivered to a series  $RLC$  circuit by a generator. This energy appears as internal energy in the resistor. What is the source of this energy?