

meters). A digital meter with such high resistance will draw off very little current when connected across a circuit element of even 1-M $\Omega$  resistance.

The precision of digital meters is exceptional, often one part in  $10^4$  ( $= 0.01\%$ ) or better. This precision is not the same as accuracy, however. A precise meter of internal resistance  $10^8 \Omega$  will not give accurate results if used to measure a voltage across a  $10^8\text{-}\Omega$  resistor—in which case it is necessary to do a calculation like that in Example 19–15.

A major aspect of this Section has been to show that whenever we make a measurement on a circuit, to some degree we affect that circuit (recall Example 19–15). This lesson is true for other types of measurement as well: whenever we make a measurement on a system, we generally affect that system in some way. On a temperature measurement, for example, the thermometer has a specific heat and can exchange heat with the system, thus altering its temperature (usually just slightly). It can be important to be able to make any needed corrections, as we saw how to do in Example 19–15.

## Summary

A device that transforms another type of energy into electrical energy is called a **source of emf**. A battery behaves like a source of emf in series with an **internal resistance**. The emf is the potential difference determined by the chemical reactions in the battery and equals the terminal voltage when no current is drawn. When a current is drawn, the voltage at the battery's terminals is less than its emf by an amount equal to the potential decrease  $Ir$  across the internal resistance.

When resistances are connected in **series** (end to end in a single linear path), the equivalent resistance is the sum of the individual resistances:

$$R_{\text{eq}} = R_1 + R_2 + \dots \quad (19-3)$$

In a series combination,  $R_{\text{eq}}$  is greater than any component resistance.

When resistors are connected in **parallel**, the reciprocal of the equivalent resistance equals the sum of the reciprocals of the individual resistances:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \quad (19-4)$$

In a parallel connection, the net resistance is less than any of the individual resistances.

**Kirchhoff's rules** are helpful in determining the currents and voltages in circuits. Kirchhoff's **junction rule** is based on conservation of electric charge and states that the sum of all currents entering any junction equals the sum of all currents leaving that junction. The second, or **loop rule**, is based on conservation of energy and states that the algebraic sum of the changes in potential around any closed path of the circuit must be zero.

When capacitors are connected in **parallel**, the equivalent capacitance is the sum of the individual capacitances:

$$C_{\text{eq}} = C_1 + C_2 + \dots \quad (19-5)$$

When capacitors are connected in **series**, the reciprocal of the equivalent capacitance equals the sum of the reciprocals of the individual capacitances:

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \quad (19-6)$$

If an **RC circuit** containing a resistance  $R$  in series with a capacitance  $C$  is connected to a dc source of emf, the voltage across the capacitor rises gradually in time characterized by the **time constant**

$$\tau = RC. \quad (19-7)$$

This is the time it takes for the voltage to reach 63% of its maximum value. A capacitor discharging through a resistor is characterized by the same time constant: in a time  $\tau = RC$ , the voltage across the capacitor drops to 37% of its initial value.

Electric shocks are caused by current passing through the body. To avoid shocks, the body must not become part of a complete circuit by allowing different parts of the body to touch objects at different potentials. Commonly, shocks are caused by one part of the body touching ground and another part touching a high electric potential.

[\*An **ammeter** measures current. An analog ammeter consists of a galvanometer and a parallel **shunt resistor** that carries most of the current. An analog **voltmeter** consists of a galvanometer and a series resistor. An ammeter is inserted *into* the circuit whose current is to be measured. A voltmeter is external, being connected in parallel to the element whose voltage is to be measured. Digital meters have greater internal resistance and affect the circuit to be measured less than do analog meters.]

## Questions

1. Explain why birds can sit on power lines safely, whereas leaning a metal ladder up against a power line to fetch a stuck kite is extremely dangerous.
2. Discuss the advantages and disadvantages of Christmas tree lights connected in parallel versus those connected in series.
3. If all you have is a 120-V line, would it be possible to light several 6-V lamps without burning them out? How?
4. Two lightbulbs of resistance  $R_1$  and  $R_2$  ( $R_2 > R_1$ ) are connected in series. Which is brighter? What if they are connected in parallel? Explain.