



FIGURE 21-42 Current in an LRC circuit as a function of frequency, showing resonance peak at $f = f_0 = (1/2\pi)\sqrt{1/LC}$.

Resonant frequency

LC circuit

EM oscillations

* 21-14 Resonance in AC Circuits

The rms current in an LRC series circuit is given by (see Eqs. 21-14, 21-15, 21-11b, and 21-12b):

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{V_{\text{rms}}}{\sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2}}. \quad (21-18)$$

Because the reactance of inductors and capacitors depends on the frequency f of the source, the current in an LRC circuit depends on frequency. From Eq. 21-18 we see that the current will be maximum at a frequency that satisfies

$$2\pi fL - \frac{1}{2\pi fC} = 0.$$

We solve this for f , and call the solution f_0 :

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}. \quad (21-19)$$

When $f = f_0$, the circuit is in resonance, and f_0 is the **resonant frequency** of the circuit. At this frequency, $X_C = X_L$, so the impedance is purely resistive. A graph of I_{rms} versus f is shown in Fig. 21-42 for particular values of R , L , and C . For smaller R compared to X_L and X_C , the resonance peak will be higher and sharper.

When R is very small, we speak of an **LC circuit**. The energy in an LC circuit oscillates, at frequency f_0 , between the inductor and the capacitor, with some being dissipated in R (some resistance is unavoidable). This is called an **LC oscillation** or an **electromagnetic oscillation**. Not only does the charge oscillate back and forth, but so does the energy, which oscillates between being stored in the electric field of the capacitor and in the magnetic field of the inductor.

Electric resonance is used in many circuits. Radio and TV sets, for example, use resonant circuits for tuning in a station. Many frequencies reach the circuit from the antenna, but a significant current flows only for frequencies at or near the resonant frequency. Either L or C is variable so that different stations can be tuned in (more on this in Chapter 22).

Summary

The **magnetic flux** passing through a loop is equal to the product of the area of the loop times the perpendicular component of the magnetic field strength:

$$\Phi_B = B_{\perp} A = BA \cos \theta. \quad (21-1)$$

If the magnetic flux through a coil of wire changes in time, an emf is induced in the coil. The magnitude of the induced emf equals the time rate of change of the magnetic flux through the loop times the number N of loops in the coil:

$$\mathcal{E} = -N \frac{\Delta \Phi_B}{\Delta t}. \quad (21-2b)$$

This is **Faraday's law of induction**.

The induced emf can produce a current whose magnetic field opposes the original change in flux (**Lenz's law**).

Faraday's law also tells us that a changing magnetic field produces an electric field; and that a straight wire of length l moving with speed v perpendicular to a magnetic field of strength B has an emf induced between its ends equal to

$$\mathcal{E} = Blv. \quad (21-3)$$

An electric **generator** changes mechanical energy into electrical energy. Its operation is based on Faraday's law: a coil of wire is made to rotate uniformly by mechanical means

in a magnetic field, and the changing flux through the coil induces a sinusoidal current, which is the output of the generator.

[*A motor, which operates in the reverse of a generator, acts like a generator in that a **back emf**, or **counter emf**, is induced in its rotating coil. Because this back emf opposes the input voltage, it can act to limit the current in a motor coil. Similarly, a generator acts somewhat like a motor in that a **counter torque** acts on its rotating coil.]

A **transformer**, which is a device to change the magnitude of an ac voltage, consists of a primary coil and a secondary coil. The changing flux due to an ac voltage in the primary coil induces an ac voltage in the secondary coil. In a 100% efficient transformer, the ratio of output to input voltages (V_S/V_P) equals the ratio of the number of turns N_S in the secondary to the number N_P in the primary:

$$\frac{V_S}{V_P} = \frac{N_S}{N_P}. \quad (21-6)$$

The ratio of secondary to primary current is in the inverse ratio of turns:

$$\frac{I_S}{I_P} = \frac{N_P}{N_S}. \quad (21-7)$$