

- * 23. A voltmeter connected across a resistor always reads *less* than the actual voltage across the resistor when the meter is not present. Explain.
- * 24. A small battery-operated flashlight requires a single 1.5-V battery. The bulb is barely glowing, but when you take the battery out and check it with a voltmeter, it registers 1.5 V. How would you explain this?

Problems

19-1 Emf and Terminal Voltage

- (I) Calculate the terminal voltage for a battery with an internal resistance of $0.900\ \Omega$ and an emf of $8.50\ \text{V}$ when the battery is connected in series with (a) an $81.0\text{-}\Omega$ resistor, and (b) an $810\text{-}\Omega$ resistor.
- (I) Four 1.5-V cells are connected in series to a $12\text{-}\Omega$ lightbulb. If the resulting current is $0.45\ \text{A}$, what is the internal resistance of each cell, assuming they are identical and neglecting the wires?
- (II) What is the internal resistance of a 12.0-V car battery whose terminal voltage drops to $8.4\ \text{V}$ when the starter draws $75\ \text{A}$? What is the resistance of the starter?
- (II) A 1.5-V dry cell can be tested by connecting it to a low-resistance ammeter. It should be able to supply at least $22\ \text{A}$. What is the internal resistance of the cell in this case, assuming it is much greater than that of the ammeter?

19-2 Resistors in Series and Parallel

In these Problems neglect the internal resistance of a battery unless the Problem refers to it.

- (I) Four $240\text{-}\Omega$ lightbulbs are connected in series. What is the total resistance of the circuit? What is their resistance if they are connected in parallel?
- (I) Three $45\text{-}\Omega$ lightbulbs and three $75\text{-}\Omega$ lightbulbs are connected in series. (a) What is the total resistance of the circuit? (b) What is their resistance if all six are wired in parallel?
- (I) A $650\text{-}\Omega$ and a $2200\text{-}\Omega$ resistor are connected in series with a 12-V battery. What is the voltage across the $2200\text{-}\Omega$ resistor?
- (I) Given only one $25\text{-}\Omega$ and one $35\text{-}\Omega$ resistor, list all possible values of resistance that can be obtained.
- (I) Suppose that you have a $680\text{-}\Omega$, a $940\text{-}\Omega$, and a $1.20\text{-k}\Omega$ resistor. What is (a) the maximum, and (b) the minimum resistance you can obtain by combining these?
- (II) Suppose that you have a 6.0-V battery and you wish to apply a voltage of only $4.0\ \text{V}$. Given an unlimited supply of $1.0\text{-}\Omega$ resistors, how could you connect them so as to make a “voltage divider” that produces a 4.0-V output for a 6.0-V input?
- (II) Three $240\text{-}\Omega$ resistors can be connected together in four different ways, making combinations of series and/or parallel circuits. What are these four ways, and what is the net resistance in each case?
- (II) A battery with an emf of $12.0\ \text{V}$ shows a terminal voltage of $11.8\ \text{V}$ when operating in a circuit with two lightbulbs rated at $3.0\ \text{W}$ (at $12.0\ \text{V}$) which are connected in parallel. What is the battery’s internal resistance?

- (II) Eight identical lights are connected in series across a 110-V line. (a) What is the voltage across each bulb? (b) If the current is $0.50\ \text{A}$, what is the resistance of each bulb, and what is the power dissipated in each?
- (II) Eight lights are connected in parallel to a 110-V source by two long leads of total resistance $1.6\ \Omega$. If $240\ \text{mA}$ flows through each bulb, what is the resistance of each, and what fraction of the total power is wasted in the leads?
- (II) Eight 7.0-W Christmas tree lights are connected in series to each other and to a 110-V source. What is the resistance of each bulb?
- (II) A close inspection of an electric circuit reveals that a $480\text{-}\Omega$ resistor was inadvertently soldered in the place where a $320\text{-}\Omega$ resistor is needed. How can this be fixed without removing anything from the existing circuit?
- (II) Determine (a) the equivalent resistance of the circuit shown in Fig. 19-39, and (b) the voltage across each resistor.

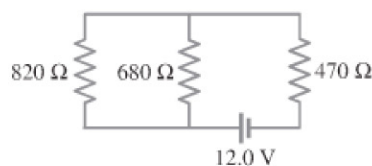


FIGURE 19-39 Problem 17.

- (II) A 75-W , 110-V bulb is connected in parallel with a 40-W , 110-V bulb. What is the net resistance?
- (III) Consider the network of resistors shown in Fig. 19-40. Answer qualitatively: (a) What happens to the voltage across each resistor when the switch S is closed? (b) What happens to the current through each when the switch is closed? (c) What happens to the power output of the battery when the switch is closed? (d) Let $R_1 = R_2 = R_3 = R_4 = 125\ \Omega$ and $V = 22.0\ \text{V}$. Determine the current through each resistor before and after closing the switch. Are your qualitative predictions confirmed?

FIGURE 19-40 Problem 19.

