

20. (III) What is the net resistance of the circuit connected to the battery in Fig. 19-41? Each resistance has $R = 2.8 \text{ k}\Omega$.

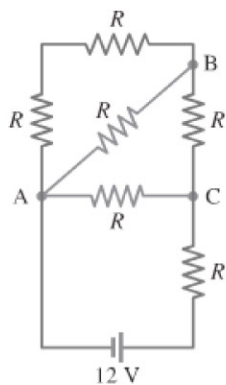


FIGURE 19-41 Problem 20.

21. (III) Three equal resistors (R) are connected to a battery as shown in Fig. 19-42. Qualitatively, what happens to (a) the voltage drop across each of these resistors, (b) the current flow through each, and (c) the terminal voltage of the battery, when the switch S is opened, after having been closed for a long time? (d) If the emf of the battery is 15.0 V , what is its terminal voltage when the switch is closed if the internal resistance is 0.50Ω and $R = 5.50 \Omega$? (e) What is the terminal voltage when the switch is open?

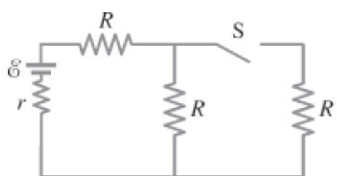


FIGURE 19-42 Problem 21.

22. (III) A $2.8\text{-k}\Omega$ and a $2.1\text{-k}\Omega$ resistor are connected in parallel; this combination is connected in series with a $1.8\text{-k}\Omega$ resistor. If each resistor is rated at $\frac{1}{2} \text{ W}$ (maximum without overheating), what is the maximum voltage that can be applied across the whole network?

19-3 Kirchhoff's Rules

23. (I) Calculate the current in the circuit of Fig. 19-43 and show that the sum of all the voltage changes around the circuit is zero.

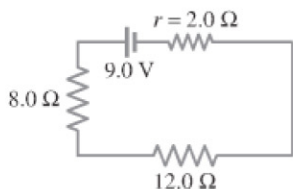


FIGURE 19-43 Problem 23.

24. (II) Determine the terminal voltage of each battery in Fig. 19-44.

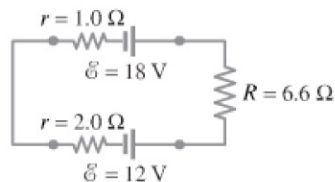


FIGURE 19-44 Problem 24.

25. (II) (a) What is the potential difference between points a and d in Fig. 19-45 (same circuit as Fig. 19-13, Example 19-8), and (b) what is the terminal voltage of each battery?

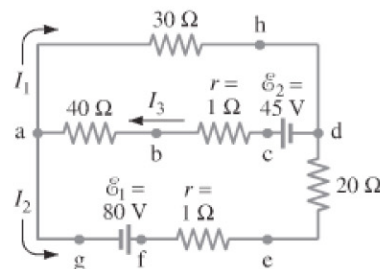


FIGURE 19-45 Problem 25.

26. (II) For the circuit shown in Fig. 19-46, find the potential difference between points a and b. Each resistor has $R = 75 \Omega$ and each battery is 1.5 V .

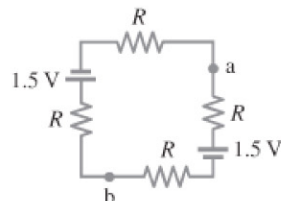


FIGURE 19-46 Problem 26.

27. (II) Determine the magnitudes and directions of the currents through R_1 and R_2 in Fig. 19-47.

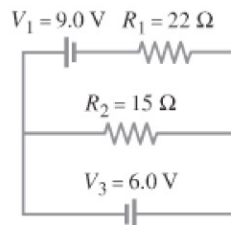


FIGURE 19-47 Problems 27 and 28.

28. (II) Repeat Problem 27, now assuming that each battery has an internal resistance $r = 1.2 \Omega$.